

Homework Assignment #5 - Due Wed. 2/20/13

- 1) A MEMS device consists of a proof mass attached to a frame with a suspension system. The bottom of the proof mass is 1mm by 1mm in size and serves as an electrode. Another electrode of the same size is located $2\mu\text{m}$ beneath it. If the proof mass can move up and down $\pm 1\mu\text{m}$ from its nominal distance to the bottom electrodes, calculate the nominal, maximum and minimum capacitance between the two electrodes. Assume that the device is in a vacuum.

Figure 1: Values of Capacitance for (1).
 $d = 2\mu\text{m}$; $\Delta d = \pm 1\mu\text{m}$; $\epsilon = 8.854\text{pF}/\text{m}$

$$C = \frac{\epsilon \times w \times L}{d - \Delta d}$$

$$C = \frac{8.854\text{pF}/\text{m} \times 1\text{mm} \times 1\text{mm}}{2\mu\text{m} - 1\mu\text{m}}$$

$$C = 8.854\text{pF}$$

(a) Maximum: $d = d - \Delta d$

$$C = \frac{\epsilon \times w \times L}{d}$$

$$C = \frac{8.854\text{pF}/\text{m} \times 1\text{mm} \times 1\text{mm}}{2\mu\text{m}}$$

$$C = 4.427\text{pF}$$

(b) Nominal: $d = d$

$$C = \frac{\epsilon \times w \times L}{d + \Delta d}$$

$$C = \frac{8.854\text{pF}/\text{m} \times 1\text{mm} \times 1\text{mm}}{2\mu\text{m} + 1\mu\text{m}}$$

$$C = 2.951\text{pF}$$

(c) Minimum: $d = d + \Delta d$

- 2) A certain MEMS capacitance has a rest (i.e. nominal) value of 3pF, a minimum value of 2pF and a maximum value of 5pF. Place it in a charge amplifier circuit that has an input voltage of 10V and a feedback capacitor (C_2) of 10pF. Calculate the amplifier output voltage (at the end of the ϕ_2 cycle) for the nominal, minimum and maximum capacitance values.

Figure 2: Amplifier Output Voltages for (2).
 $V_{in} = 10\text{V}$; $C_2 = 10\text{pF}$; After ϕ_2 , $V_{out} = \frac{-C_s V_{in}}{C_2}$

$$C_s = 2\text{pF}$$

$$V_{out} = \frac{-C_s V_{in}}{C_2} = \frac{-2\text{pF} \times 10\text{V}}{10\text{pF}}$$

$$V_{out} = -2\text{V}$$

(a) V_{out} for C_{min}

$$C_s = 3\text{pF}$$

$$V_{out} = \frac{-C_s V_{in}}{C_2} = \frac{-3\text{pF} \times 10\text{V}}{10\text{pF}}$$

$$V_{out} = -3\text{V}$$

(b) V_{out} for C_{nom}

$$C_s = 5\text{pF}$$

$$V_{out} = \frac{-C_s V_{in}}{C_2} = \frac{-5\text{pF} \times 10\text{V}}{10\text{pF}}$$

$$V_{out} = -5\text{V}$$

(c) V_{out} for C_{max}

- 3) For the MEMS capacitance in (2) place it in a 5V “fast” CMOS ring oscillator circuit with both resistors being $100\text{k}\Omega$. What is the output frequency for C_{min} , C_{nom} and C_{max} ?

Figure 3: Output Frequencies for (3).
 $t = -RC \ln^{1/3}$; $f = 1/T$; $T = 2t$; $f = \frac{0.455}{RC}$

$$C = 2\text{pF}; R = 100\text{k}\Omega$$

$$f = \frac{0.455}{RC} = \frac{0.455}{100\text{k}\Omega 2\text{pF}}$$

$$f = 2.275\text{MHz}$$

(a) f_o for C_{min}

$$C = 3\text{pF}; R = 100\text{k}\Omega$$

$$f = \frac{0.455}{RC} = \frac{0.455}{100\text{k}\Omega 3\text{pF}}$$

$$f = 1.517\text{MHz}$$

(b) f_o for C_{nom}

$$C = 5\text{pF}; R = 100\text{k}\Omega$$


$$f = \frac{0.455}{RC} = \frac{0.455}{100\text{k}\Omega 5\text{pF}}$$

$$f = 910\text{kHz}$$

(c) f_o for C_{max}

- 4) If two MEMS capacitances from (2) are placed in a capacitive AC voltage divider to realize a differential capacitive sensor configuration, with the input voltage having an amplitude of 10V, what is the output voltage amplitude for each case?

Figure 4: Output Voltage Amplitude for each case in (4).

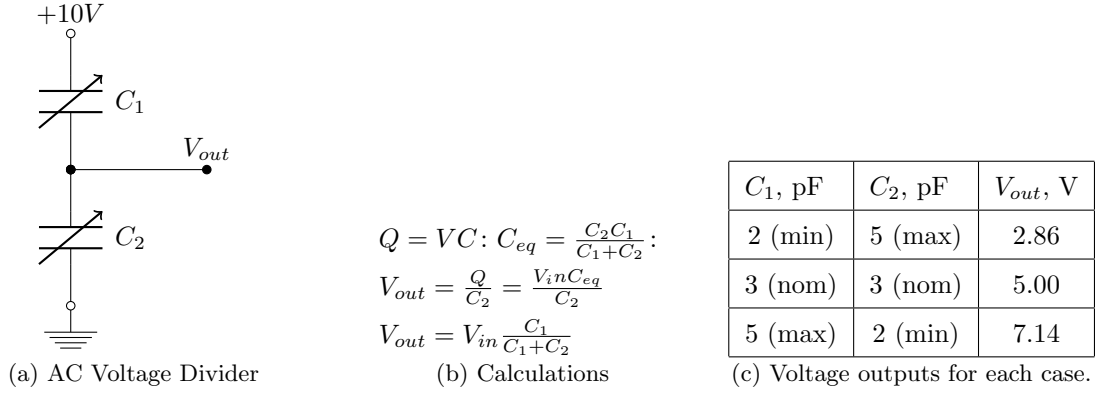

- 5) If the MEMS capacitance from (2) is placed in a switched-capacitor circuit that is switched at 250KHz, what is the value of the equivalent resistance for the nominal, minimum and maximum capacitance values?

Figure 5: Equivalent Resistances for (5).

$$f_{switch} = 250kHz$$

$$i = \frac{\delta q}{\delta t} = \frac{Q}{T} = \frac{CV_{in}}{T} = Cf_{switch}V_{in}$$

$$\Rightarrow R = \frac{V}{i} = \frac{1}{Cf_{switch}}$$

$C = 2pF$
 $R = \frac{1}{Cf_{switch}} = \frac{1}{2pF \times 250kHz}$
 $R = 2M\Omega$
 (a) R for C_{min}

$C = 3pF$
 $R = \frac{1}{Cf_{switch}} = \frac{1}{3pF \times 250kHz}$
 $R = 1.333M\Omega$
 (b) R for C_{nom}

$C = 5pF$
 $R = \frac{1}{Cf_{switch}} = \frac{1}{5pF \times 250kHz}$
 $R = 800k\Omega$
 (c) R for C_{max}

- 6) If the MEMS device in (2) is placed in an RC phase delay circuit, where $R = 250k\Omega$, what is the phase delay in μs for the nominal, minimum and maximum capacitance values?

Figure 6: Phase Delay for (6).

$$V_{out} = \frac{V_{in}}{s} \frac{1/sC}{R + 1/sC} = \frac{V_{in}}{s} - \frac{V_{in}}{s + 1/RC}$$

$$V_{out}(t) = V_{in}(1 - e^{-t/RC})$$

$$t: V_{out} = V_{in}/2 \rightarrow V_{in}/2 = V_{in}(1 - e^{-t/RC})$$

$$1/2 = 1 - e^{-t/RC} \rightarrow t = -RC \ln 1/2$$

$$t = 0.693RC$$

$C = 2pF: R = 250k\Omega$
 $t = 0.692(2pf)(250k\Omega)$
 $t = 0.346\mu s$
 (a) Phase delay for C_{min}

$C = 3pF: R = 250k\Omega$
 $t = 0.692(3pf)(250k\Omega)$
 $t = 0.520\mu s$
 (b) Phase delay for C_{nom}

$C = 5pF: R = 250k\Omega$
 $t = 0.692(5pf)(250k\Omega)$
 $t = 0.866\mu s$
 (c) Phase delay for C_{max}