
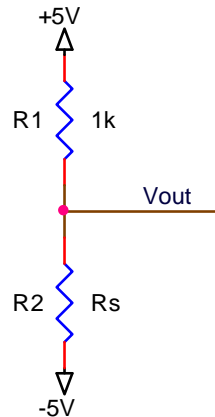


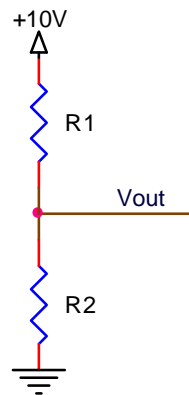- 1) An unbuffered resistive sensor, R_s , is in the circuit shown below, where $500\Omega \leq R_s \leq 1.5k\Omega$. What is V_{out} for the minimum, mid range and maximum resistance values of the sensor?




- 2) For the differential resistance sensor shown below, where $R_1 = 1k\Omega + \Delta R$, $R_2 = 1k\Omega - \Delta R$, and $0\Omega \leq \Delta R \leq 100\Omega$, calculate the minimum and maximum V_{out} .



- 3) A rectangular resistive temperature sensor (5mm long, $50\mu\text{m}$ wide and $1\mu\text{m}$ thick), where current flows through the length of the sensor, is made of a material with a resistivity of $5 \times 10^{-6} \Omega\text{-cm}$ at 0°C , and a TCR of $5 \times 10^{-3} (^\circ\text{C})^{-1}$. What is the approximate resistance at 0°C and 100°C ?
- 4) A certain metal strain gauge has a nominal resistance of $10k\Omega$ and a gauge factor of 1.8. If it experiences a 1% axial strain, what does the resistance become?
- 5) If the strain gauge in (4) experiences a -1% axial strain, what does the resistance become?

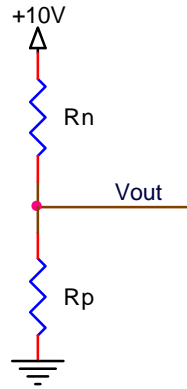- 6) A polysilicon differential piezoresistive sensor is connected to a 10V source as shown below, where R_n is a N-type piezoresistor and R_p is a P-type piezoresistor. With no strain on the piezoresistors, $R_n = R_p = 1\text{k}\Omega$. Calculate V_{out} for no strain. If R_n has a GF of -30 and R_p has a GF of +30, and both piezoresistors experience a 0.2% axial strain, calculate V_{out} .



- 7) If four piezoresistors from problem (6) are connected in a Wheatstone bridge configuration, as shown below, calculate $V_{out} = V_2 - V_1$ for all resistors experiencing a 0.1% axial strain.

